




IO male pin output soldered into circuit board.




Resistor. By convention they are all 10kΩ, but they only need to be equal for each channel.

Micro-USB port

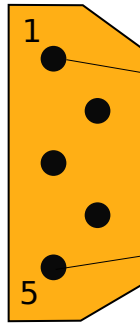

+ 5V DC

-

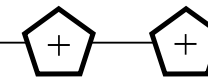

Right Channel circuit

Servo output signal pin



8

7

6

5

LM358N Dual OpAmp Chip

1

2


3

4

Servo output signal pin



Left Channel circuit

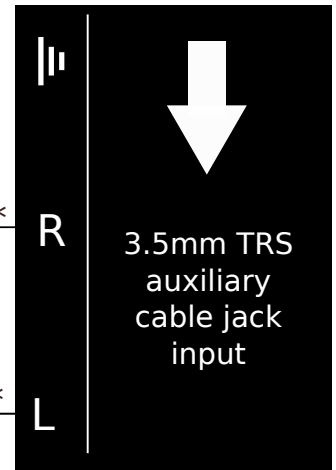

* These connections are interchangeable, just that it changes the output terminals.